

EE2001: CIRCUIT ANALYSIS

Tutorial 7 Solutions

(Power Factor)

{ Note : This tutorial will be preceded by Quiz Test }

7.1

(a) Find the original power factor seen by the source in problem 6.4.


$$S_T = 6.395 + j 0.233 \text{ kVA}$$

(Inductive load)

$$\text{pf} = \cos \left(\tan^{-1} \frac{0.233}{6.395} \right) = 0.9993$$

$$\approx 1$$

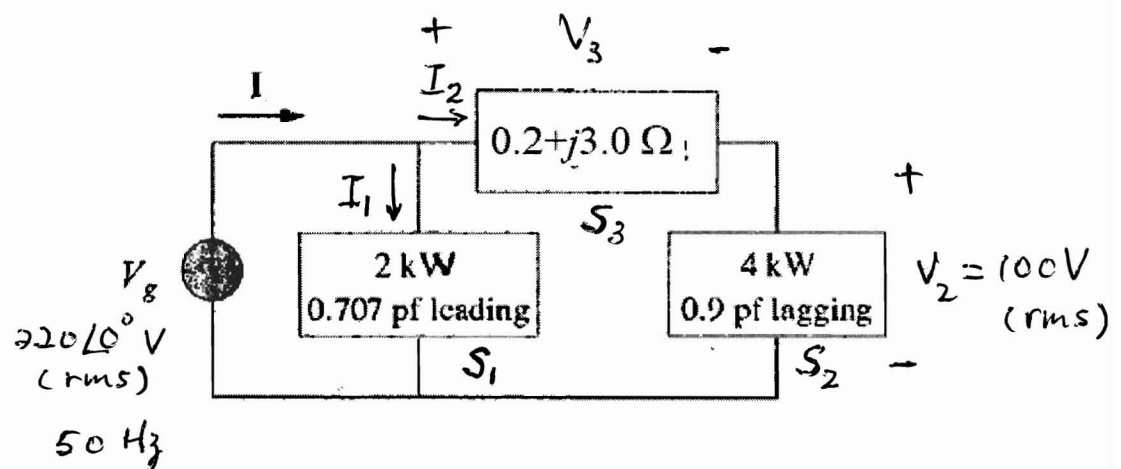(b) Determine the power factor of the network on addition of the new load.



From Problem 6.4,

$$I_2 = 40 - j19.37 \text{ A}$$

$$S_3 = V_3 I_2^*$$

$$= (0.2 + j3) I_2 \cdot I_2^*$$

$$= (0.2 + j3) (40 - j19.37) (40 + j19.37)$$

$$= (0.2 + j3) (40^2 + 19.37^2)$$

$$= 395.04 + j5925.6 \text{ VA}$$

$$S_T = S_1 + S_2 + S_3$$

$$= (2 - j2) \cdot 10^3 + (4 + j1.937) \cdot 10^3 \\ + 395.04 + j5925.6$$

$$= 6.395 + j5.862 \text{ kVA (Inductive load)}$$

$$\text{pf} = \cos \left(\tan^{-1} \frac{5.862}{6.395} \right) = 0.7372$$

lagging.

Power factor angle is

$$\theta = \tan^{-1} \frac{5.862}{6.395} = 42.5^\circ$$

~~100~~

(c)

To raise the power factor from 0.7375 lagging to unity.

$$\theta = 42.5^\circ \longrightarrow \theta_c = 0^\circ$$

Connect a capacitor parallel to the loads, hence

$$\begin{aligned} Q_c &= P (\tan \theta - \tan \theta_c) \\ &= 6395 (\tan 42.5^\circ - \tan 0^\circ) \\ &= 5859.9 \text{ VAR} \end{aligned}$$

$$\begin{aligned} C &= \frac{Q_c}{\omega V_{rms}^2} \\ &= \frac{5859.9}{2\pi \cdot 50 \cdot 220^2} \\ &= 0.4 \text{ mF} \end{aligned}$$

~~122~~